

Electrical Power Engineering (2)

Code: EP2207

Lecture: 4

Tutorial: 4

Total: 8

Dr. Ahmed Mohamed Azmy

Department of Electrical Power and Machine Engineering

Tanta University - Egypt




Faculty of
Engineering



Tanta University

Performance of long transmission lines

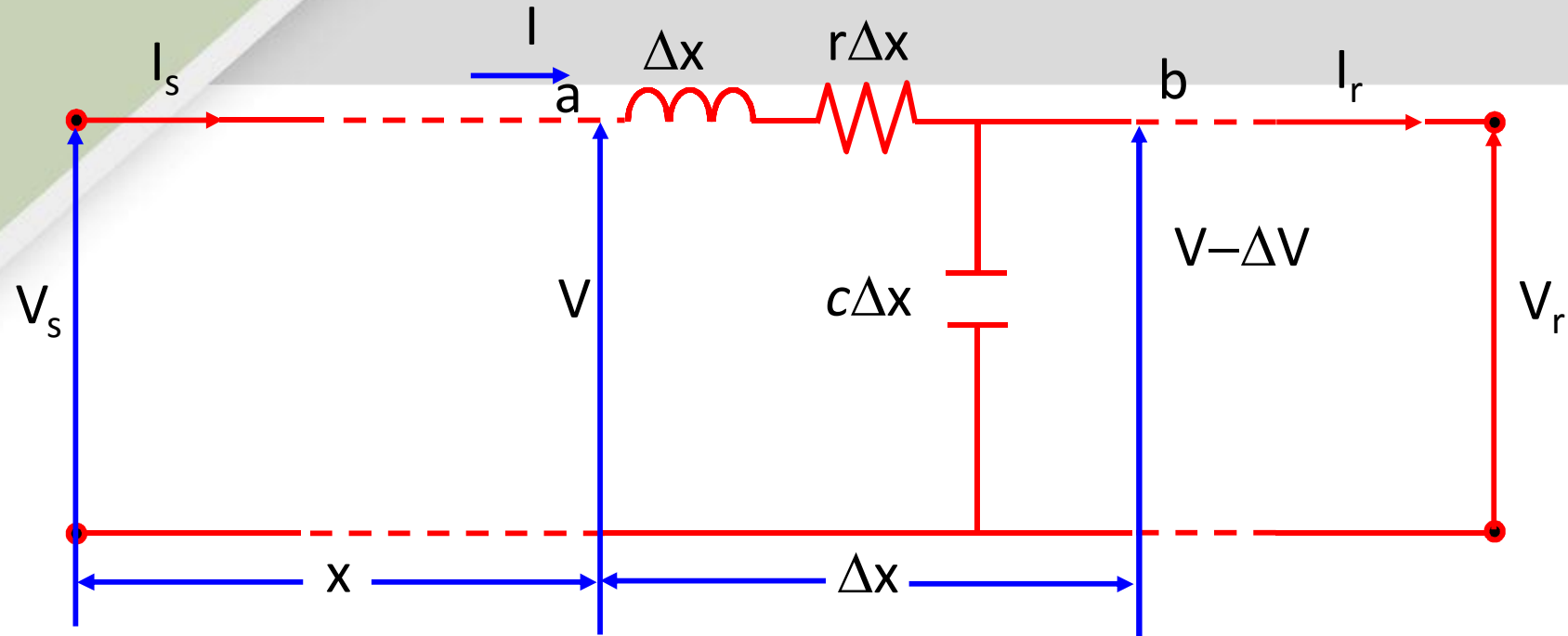

r : is the resistance per unit length of the line

l : is inductance per unit length of the line

z : is impedance per unit length of the line

c : is capacitance per unit length of the line

y : is admittance per unit length of the line

Performance of long transmission lines

θ : is the propagation constant معامل الانتشار

$$\theta = \sqrt{zy}$$

$$\theta = \alpha + j \beta$$

α : is the attenuation constant معامل التوهين

β : is the phase constant

Z_o : is the characteristic impedance of the line

$$Z_o = \sqrt{\frac{z}{y}}$$

Performance of long transmission lines

$$V_s = \cosh(\theta) V_r + Z \frac{\sinh(\theta)}{\theta} I_r$$

$$I_s = Y \frac{\sinh(\theta)}{\theta} V_r + \cosh(\theta) I_r$$

$$A = D = \cosh(\theta)$$

$$B = Z \frac{\sinh(\theta)}{\theta}$$

$$C = Y \frac{\sinh(\theta)}{\theta}$$

Equivalent Π and T of long TL

Nominal T representation

$$A = D = 1 + \frac{Z'Y'}{2} = \cosh(\theta)$$

$$B = Z' \left(1 + \frac{Z'Y'}{4} \right) = Z \frac{\sinh(\theta)}{\theta}$$

$$C = Y' = Y \frac{\sinh(\theta)}{\theta}$$

Equivalent Π and T of long TL

Nominal T representation

$$\frac{Z'Y'}{2} = \cosh(\theta) - 1$$

$$\frac{Z'}{2} \left(Y \frac{\sinh(\theta)}{\theta} \right) = \cosh(\theta) - 1$$

$$\frac{Z'}{2} = \left(\frac{\cosh(\theta) - 1}{\sinh(\theta)} \right) \frac{\theta}{Y}$$

$$A = D = 1 + \frac{Z'Y'}{2} = \cosh(\theta)$$

$$Y' = Y \frac{\sinh(\theta)}{\theta}$$

$$\frac{Z'}{2} = \frac{\theta}{Y} \left(\frac{\tanh\left(\frac{\theta}{2}\right)}{\frac{\theta}{2}} \right) \frac{\theta}{2} = \frac{\theta^2}{2Y} \left(\frac{\tanh\left(\frac{\theta}{2}\right)}{\frac{\theta}{2}} \right)$$

$$Z' = Z \left(\frac{\tanh\left(\frac{\theta}{2}\right)}{\frac{\theta}{2}} \right)$$

Equivalent Π and T of long TL


Nominal Π representation

$$A = D = 1 + \frac{Z'Y'}{2} = \cosh(\theta)$$

$$B = Z' = Z \frac{\sinh(\theta)}{\theta}$$


$$Y' = Y \left(\frac{\tanh\left(\frac{\theta}{2}\right)}{\frac{\theta}{2}} \right)$$

General Constants of cascaded TL

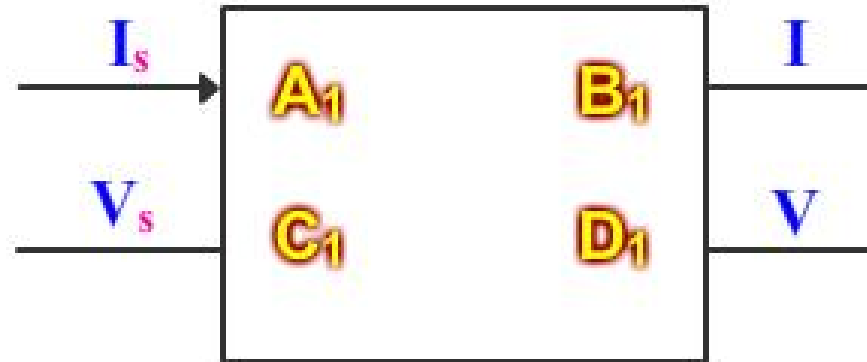

$$V_s = A_1 V + B_1 I$$


$$I_s = C_1 V + D_1 I$$

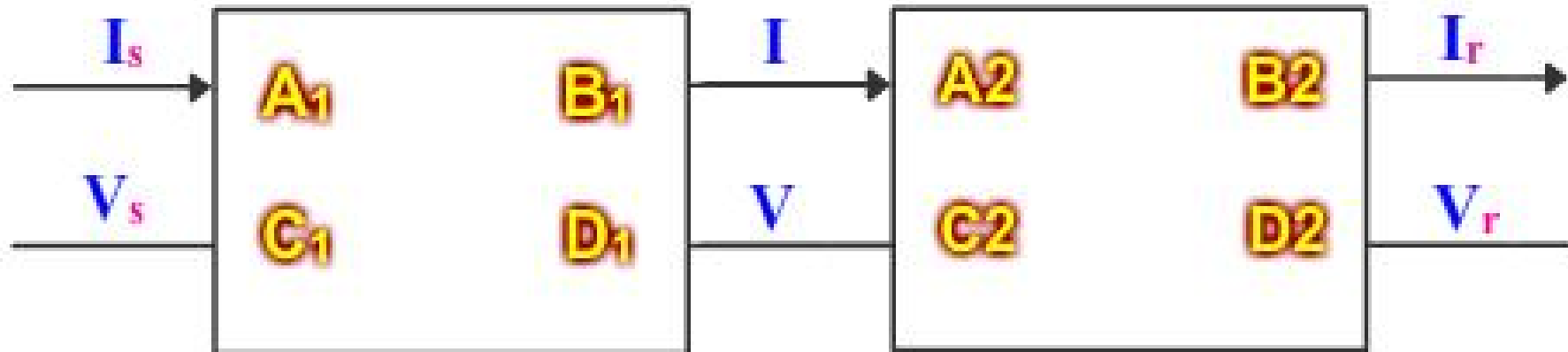

$$V = A_2 V_r + B_2 I_r$$


$$I = C_2 V_r + D_2 I_r$$

General Constants of cascaded TL

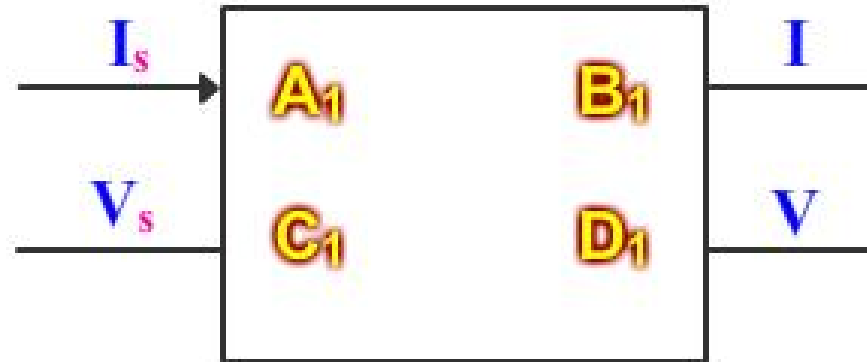

$$V_s = A_1 V + B_1 I$$

$$I_s = C_1 V + D_1 I$$

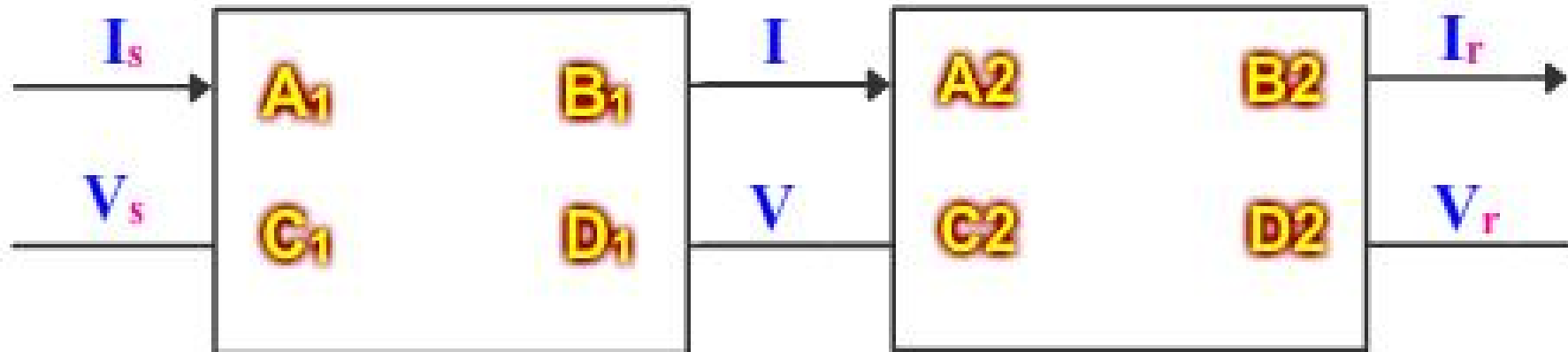

$$V = A_2 V_r + B_2 I_r$$

$$I = C_2 V_r + D_2 I_r$$

General Constants of cascaded TL


$$\begin{bmatrix} \mathbf{V} \\ \mathbf{I} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_2 & \mathbf{B}_2 \\ \mathbf{C}_2 & \mathbf{D}_2 \end{bmatrix} \begin{bmatrix} \mathbf{V}_r \\ \mathbf{I}_r \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{V}_s \\ \mathbf{I}_s \end{bmatrix} = \begin{bmatrix} \mathbf{A}_1 & \mathbf{B}_1 \\ \mathbf{C}_1 & \mathbf{D}_1 \end{bmatrix} \begin{bmatrix} \mathbf{V} \\ \mathbf{I} \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{V}_s \\ \mathbf{I}_s \end{bmatrix} = \begin{bmatrix} \mathbf{A}_1 & \mathbf{B}_1 \\ \mathbf{C}_1 & \mathbf{D}_1 \end{bmatrix} \begin{bmatrix} \mathbf{A}_2 & \mathbf{B}_2 \\ \mathbf{C}_2 & \mathbf{D}_2 \end{bmatrix} \begin{bmatrix} \mathbf{V}_r \\ \mathbf{I}_r \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{V}_s \\ \mathbf{I}_s \end{bmatrix} = \begin{bmatrix} \mathbf{A}_1\mathbf{A}_2 + \mathbf{B}_1\mathbf{C}_2 & \mathbf{A}_1\mathbf{B}_2 + \mathbf{B}_1\mathbf{D}_2 \\ \mathbf{C}_1\mathbf{A}_2 + \mathbf{D}_1\mathbf{C}_2 & \mathbf{C}_1\mathbf{B}_2 + \mathbf{D}_1\mathbf{D}_2 \end{bmatrix} \begin{bmatrix} \mathbf{V}_r \\ \mathbf{I}_r \end{bmatrix}$$

General Constants of cascaded TL

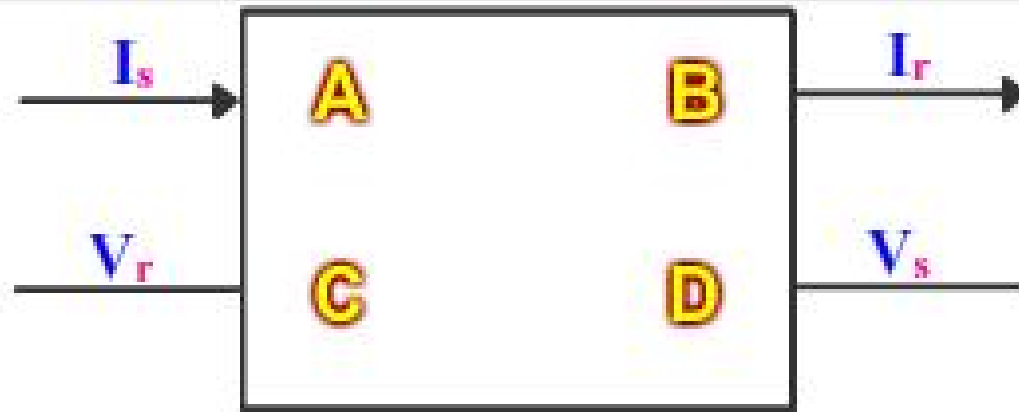


$$A = A_1 A_2 + B_1 C_2$$

$$B = A_1 B_2 + B_1 D_2$$

$$C = C_1 A_2 + D_1 C_2$$

$$D = C_1 B_2 + D_1 D_2$$

General Constants of Parallel TL

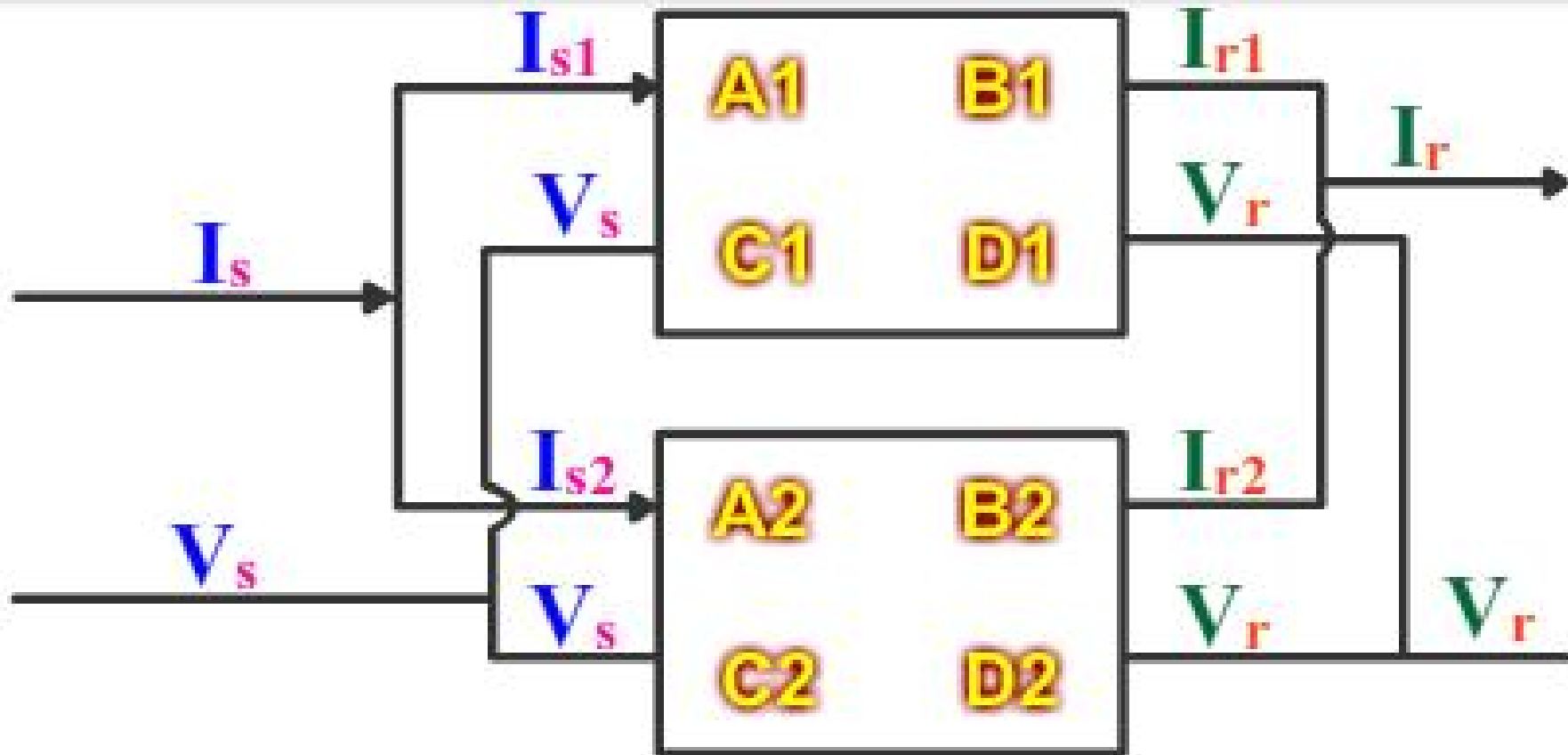

$$A_1 V_r + B_1 I_{r1} = A_2 V_r + B_2 I_{r2}$$

$$I_{r2} = I_r - I_{r1}$$

General Constants of Parallel TL

$$A_1 V_r + B_1 I_{r1} = A_2 V_r + B_2 I_{r2}$$


$$I_{r2} = I_r - I_{r1}$$

Thus,

$$V_s = \frac{A_1 B_2 + B_1 A_2}{B_1 + B_2} V_r + \frac{B_1 B_2}{B_1 + B_2} I_r$$

$$I_s = C_1 + C_2 + \frac{(A_2 - A_1)(D_1 - D_2)}{B_1 + B_2} V_r + \frac{B_1 D_2 + B_2 D_1}{B_1 + B_2} I_r$$

General Constants of Parallel TL

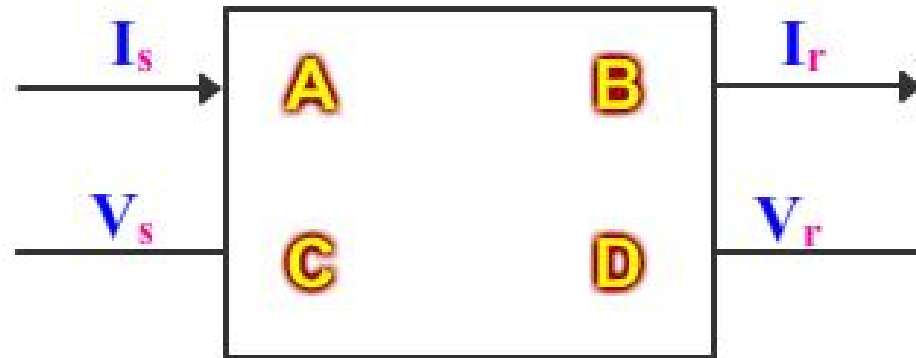

$$A = \frac{A_1 B_2 + B_1 A_2}{B_1 + B_2}$$

$$B = \frac{B_1 B_2}{B_1 + B_2}$$

$$C = C_1 + C_2 + \frac{(A_2 - A_1)(D_1 - D_2)}{B_1 + B_2}$$

$$D = \frac{B_1 D_2 + B_2 D_1}{B_1 + B_2}$$